
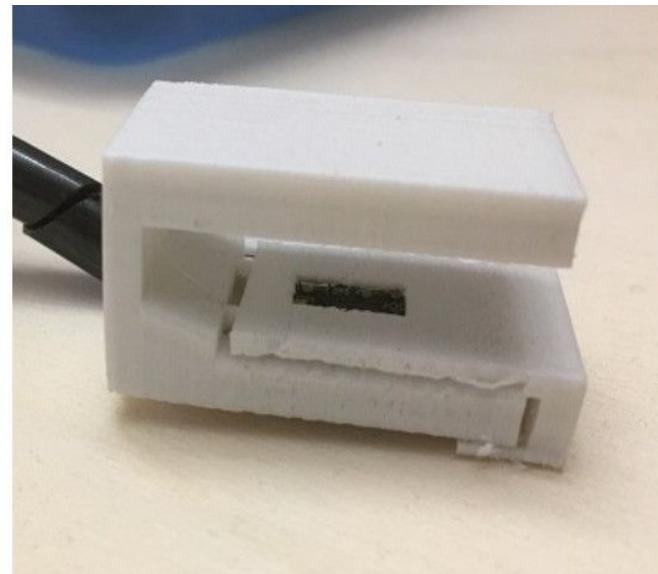




# Topics Today

- Circuit Design
  - Pulsed Current Source Design for controlling the diode
- 3D CAD Designs for Clip


# Clip Designs 1

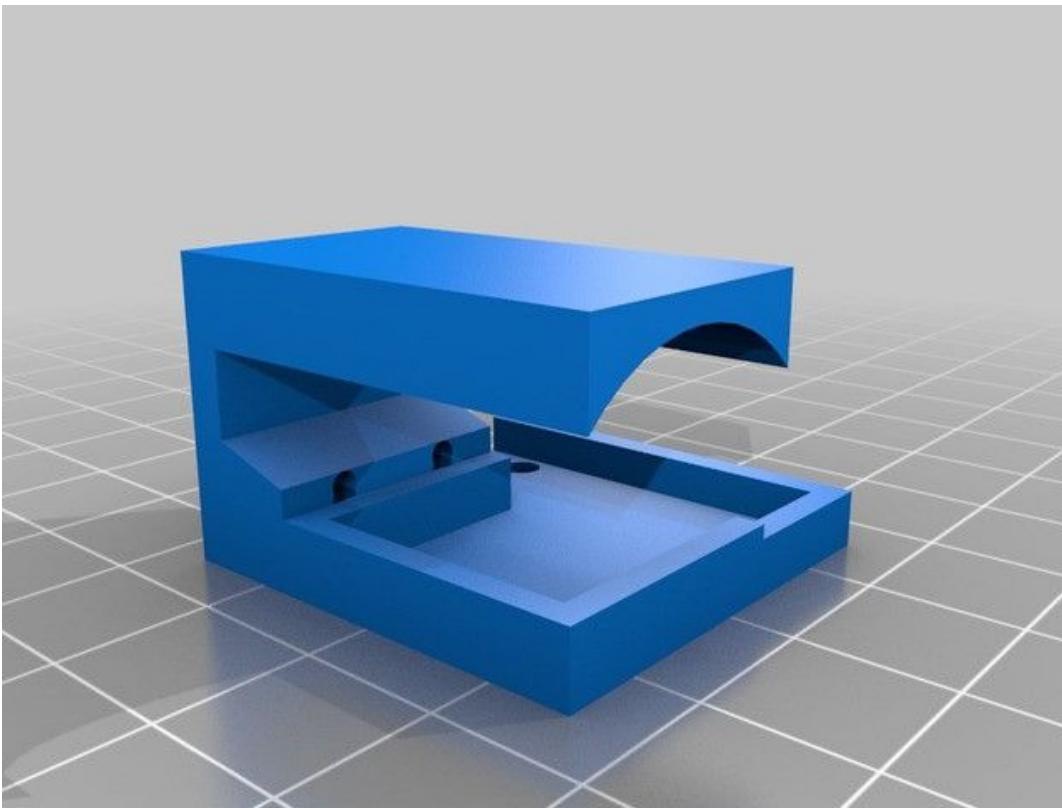

# Clip Design 2

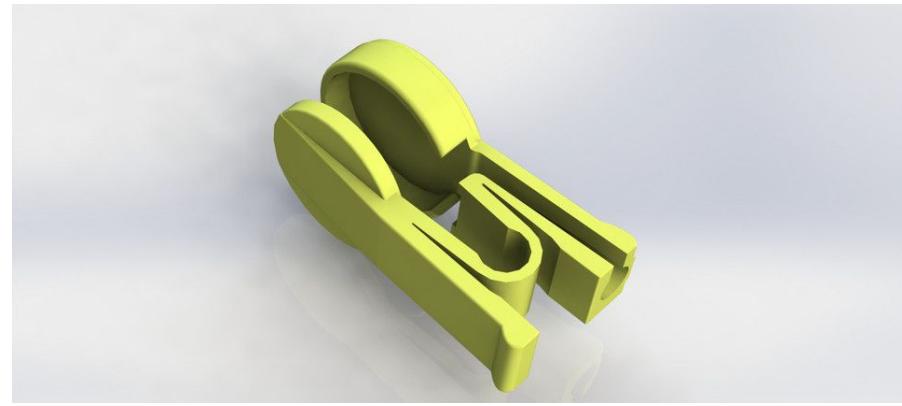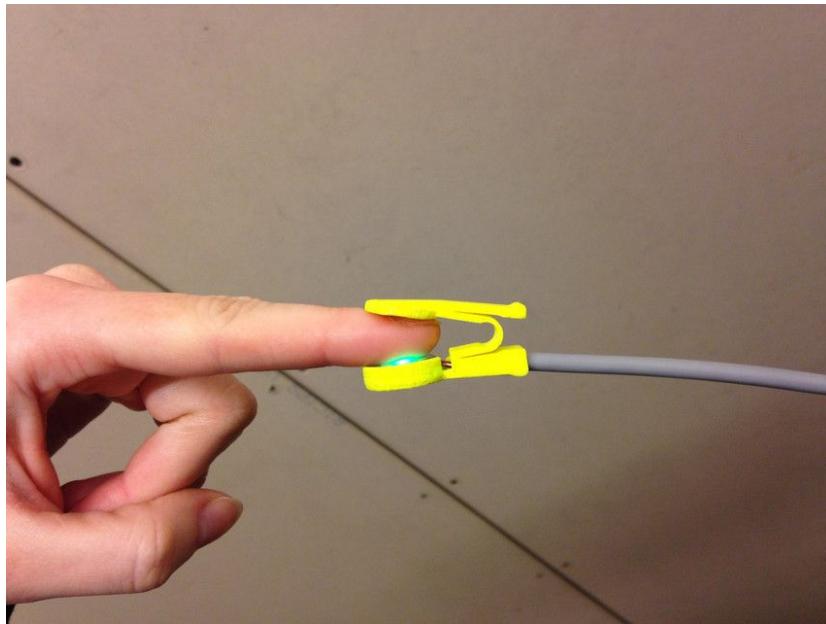

# Current to Voltage Converter

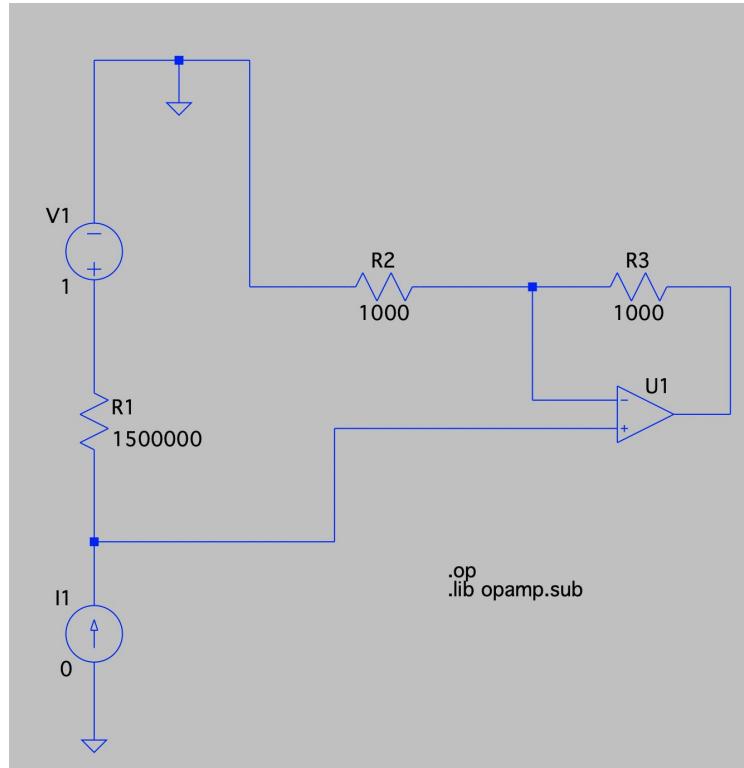

# Variable Current Source

